

Lab 3 Tutorial

32-bit ALU Design

OVERVIEW

i In this lab we will implement, test, and simulate a 32-bit Arithmetic Logic Unit (ALU) capable of performing the following operations:

Operation Name	ALU-Op		Operation Performed
	<i>Neg/Tsel</i>	<i>ALU-Select</i>	
AND (Logical)	0	00	Result \leq a AND b
Or (Logical)	0	01	Result \leq a OR b
ADD	0	10	Result \leq a + b
SUB	1	10	Result \leq a – b
ROL	1	00	Result \leq a \ll 1
ROR	1	01	Result \leq a \gg 1

i As per the lab specifications outlined in the lab manual:

*“The addition and subtraction operations should be performed using a structural approach (i.e, **A+B** and **A-B** VHDL statements are not acceptable).”*

Please refer to the lab manual for more information on this.

i We will design the following components to complete this lab:

1. 1-bit full adder.
2. 4-bit adder built using four 1-bit full adders.
3. 16-bit adder built using four 4-bit adders.

4. 32-bit adder/subtractor built using two 16-bit adders. We will use this 32-bit adder/subtractor to implement the addition and subtraction operations performed by the 32-bit ALU.
5. 32-bit ALU.

Only the simulation waveforms for the 32-bit ALU will be provided in this tutorial.

MAKE SURE THAT YOU CHOOSE THE “EP4CE115F29C7” DEVICE IN THE PROJECT WIZARD.



PROCEDURE

1. 1-bit Full Adder (fulladd.vhd)

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4
5  entity fulladd is
6  port(
7      Cin, x, y : in  std_logic;
8      s, Cout   : out std_logic
9  );
10 end fulladd;
11
12 architecture Behavior of fulladd is
13 begin
14     s <= x xor y xor Cin;
15     Cout <= (x and y) or (Cin and x) or (Cin and y);
16 end Behavior;
17

```

  

equivalent

$((x \text{ xor } y) \text{ and } cin) \text{ or } (x \text{ and } y)$

2. 4-bit Adder (adder4.vhd)

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4
5  entity adder4 is
6  port(
7      Cin      : in std_logic;
8      X,Y      : in std_logic_vector(3 downto 0);
9      S        : out std_logic_vector(3 downto 0);
10     Cout     : out std_logic
11 );
12 end adder4;

```


Portmap goes in order
(Cin, x, y, S, Cout)

```

13
14 architecture Behavior of adder4 is
15     component fulladd
16     port(
17         Cin, x, y : in std_logic;
18         s, Cout   : out std_logic
19     );
20     end component;
21
22     signal C : std_logic_vector (1 to 3);
23 begin
24     stage0: fulladd port map (Cin, X(0), Y(0), S(0), C(1));
25     stage1: fulladd port map (C(1), X(1), Y(1), S(1), C(2));
26     stage2: fulladd port map (C(2), X(2), Y(2), S(2), C(3));
27     stage3: fulladd port map (C(3), X(3), Y(3), S(3), Cout);
28 end Behavior;
29

```

 Taking component
1 bit full adder (Prew state)
to make 4-bit full adder



4-bit Ripple Carry Adder

3. 16-bit Adder (adder16.vhd)

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4
5  entity adder16 is
6  port(
7      Cin      : in std_logic;
8      X,Y      : in std_logic_vector(15 downto 0);
9      S        : out std_logic_vector(15 downto 0);
10     Cout     : out std_logic
11 );
12 end adder16;
13
14 architecture Behavior of adder16 is
15     component adder4
16     port(
17         Cin      : in std_logic;
18         X,Y      : in std_logic_vector(3 downto 0);
19         S        : out std_logic_vector(3 downto 0);
20         Cout     : out std_logic
21     );
22     end component;
23
24     signal C : std_logic_vector (1 to 3);
25 begin
26     stage0: adder4 port map (Cin, 4 X(3 downto 0), Y(3 downto 0), S(3 downto 0), C(1));
27     stage1: adder4 port map (C(1), 8 X(7 downto 4), Y(7 downto 4), S(7 downto 4), C(2));
28     stage2: adder4 port map (C(2), 12 X(11 downto 8), Y(11 downto 8), S(11 downto 8), C(3));
29     stage3: adder4 port map (C(3), 16 X(15 downto 12), Y(15 downto 12), S(15 downto 12),
30     Cout);
31 end Behavior;

```

4. 32-bit Adder/Subtractor (adder32.vhd)

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4
5  entity adder32 is
6  port(
7      Cin      : in std_logic;
8      X,Y      : in std_logic_vector(31 downto 0);
9      S        : out std_logic_vector(31 downto 0);
10     Cout     : out std_logic
11 );
12 end adder32;
13
14 architecture Behavior of adder32 is
15     component adder16
16     port(
17         Cin      : in std_logic;
18         X,Y      : in std_logic_vector(15 downto 0);
19         S        : out std_logic_vector(15 downto 0);
20         Cout     : out std_logic
21     );
22     end component;
23
24     signal C : std_logic;
25 begin
26     stage0: adder16 port map (Cin, X(15 downto 0), Y(15 downto 0), S(15 downto 0),
27         C);
28     stage1: adder16 port map (C, X(31 downto 16), Y(31 downto 16), S(31 downto 16), Cout);
29 end Behavior;

```

 


Figure 1: 32-bit ALU

5. 32-bit ALU (alu.vhd)

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5  use ieee.numeric_std.all;
6
7  entity alu is
8  port(
9      a      : in  std_logic_vector(31 downto 0);
10     b      : in  std_logic_vector(31 downto 0);
11     op      : in  std_logic_vector(2 downto 0);
12     result  : out std_logic_vector(31 downto 0);
13     zero    : out std_logic;
14     cout    : out std_logic
15 );
16 end alu;
17
18 architecture Behavior of alu is
19     component adder32
20     port(
21         Cin      : in std_logic;
22         X,Y      : in std_logic_vector(31 downto 0);
23         S        : out std_logic_vector(31 downto 0);
24         Cout     : out std_logic
25     );
26 end component;
27
28     signal result_s: std_logic_vector(31 downto 0) := (others => '0');
29     signal result_add: std_logic_vector(31 downto 0) := (others => '0');
30     signal result_sub: std_logic_vector(31 downto 0) := (others => '0');
31     signal cout_s : std_logic := '0';
32     signal cout_add : std_logic := '0';
33     signal cout_sub : std_logic := '0';
34     signal zero_s : std_logic;
35
36 begin
37     add0 : adder32 port map (op(2), a, b, result_add, cout_add);
38     sub0 : adder32 port map (op(2), a, not b, result_sub, cout_sub);
39
40     process (a, b, op)
41     begin
42         case (op) is
43             when "000" => -- "000" a and b
44                 result_s <= a and b;
45                 cout_s <= '0';
46             when "001" => -- "001" a or b
47                 result_s <= a or b;
48                 cout_s <= '0';
49             when "010" => -- "010" a + b
50                 result_s <= result_add;
51                 cout_s <= cout_add;
52             when "011" => -- "011" b
53                 result_s <= b;
54                 cout_s <= '0';
55             when "110" => -- "110" a - b
56                 result_s <= result_sub;
57                 cout_s <= cout_sub;
58             when "100" => -- a sll 1
59                 result_s <= a(30 downto 0) & '0';
60                 cout_s <= a(31);
61             when "101" => -- a srl 1

```

 


Figure 1: 32-bit ALU

Page 1 of 2

Revision: ALU

Operation Name	ALU-Op		Operation Performed
	Neg/Tsel	ALU-Select	
AND (Logical)	0	00	Result <= a AND b
Or (Logical)	0	01	Result <= a OR b
ADD	0	10	Result <= a + b
SUB	1	10	Result <= a – b
ROL	1	00	Result <= a << 1
ROR	1	01	Result <= a >> 1

```
62         result_s <= '0' & a(31 downto 1);
63         cout_s <= '0';
64         when others =>
65             result_s <= a;
66             cout_s <= '0';
67         end case;
68
69         case (result_s) is
70             when (others => '0') =>
71                 zero_s <= '1';
72             when others =>
73                 zero_s <= '0';
74         end case;
75     end process;
76
77     result <= result_s;
78     cout <= cout_s;
79     zero <= zero_s;
80 end Behavior;
81
82
```

